



Change RF Final Amp screen bypass to 0.0015uF (originally 0.05).  
 Tune for CW Mode 2.5 mA grid, 120 mA plate.  
 Tune for AM Mode 2.5 mA grid, 70 mA plate.

Replace R34 with 8H, 150 mA, High Voltage choke.

DX-60 Speech Amp Modifications  
 Circuit by Ed,KS3K, 1996  
 Drawing by S. Ickes, WB3HUZ, Feb 1997